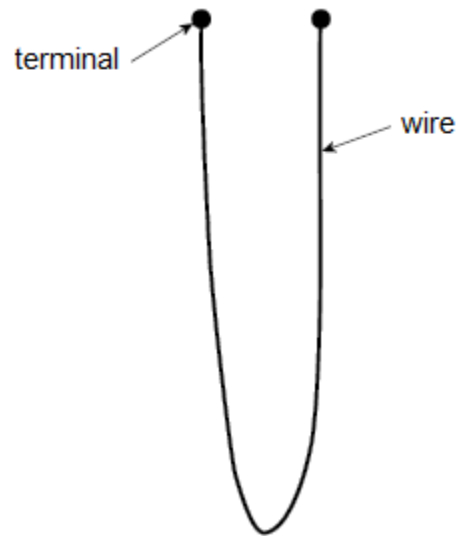


1

A wire probe is used to measure the rate of corrosion in a pipe carrying a corrosive liquid. The probe is made from the same metal as the pipe. **Figure 1** shows the probe. The rate of corrosion of the wire in the probe is the same as in the pipe.

Figure 1



- (a) The wire in an unused probe has a resistance of 0.070Ω and a length of 0.50 m .


Calculate the diameter of the wire.

resistivity of metal in the wire = $9.7 \times 10^{-8} \Omega \text{ m}$

diameter = _____ m

(3)

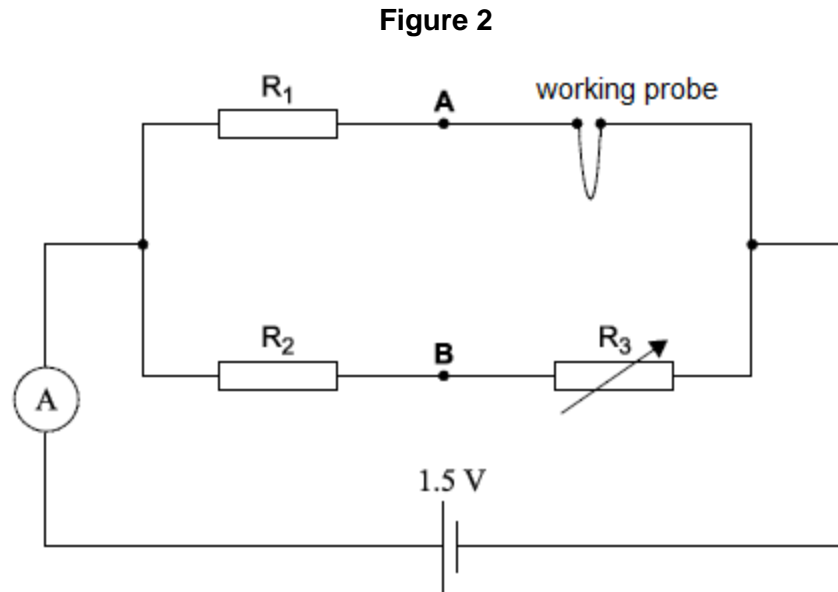- (b) In order to measure the resistance of a used working probe, it is connected in the circuit shown in **Figure 2**.



When R_3 is adjusted to a particular value the current in the cell is 0.66 A.

Calculate the total resistance of the circuit.

You may assume that the cell has a negligible internal resistance.

resistance = _____ Ω

(1)

- (c) The resistance of R_2 is 22Ω and the resistance of R_3 is 1.2Ω .

Calculate the current in R_3 .

current = _____ A

(1)

- (d) Calculate the resistance of the probe when the resistance of R_1 is 2.4Ω .

resistance = _____ Ω

(3)

- (e) Calculate the percentage change in the diameter of the probe when its resistance increases by 1.6 %.

percentage change = _____ %

(2)

- (f) A voltmeter is connected between points **A** and **B** in the circuit and R_3 stays at 1.2Ω .


Explain, without calculation, why the reading on the voltmeter does not change when the cell in the circuit is replaced with another cell of the same emf but a significant internal resistance.

(2)

(Total 12 marks)

2

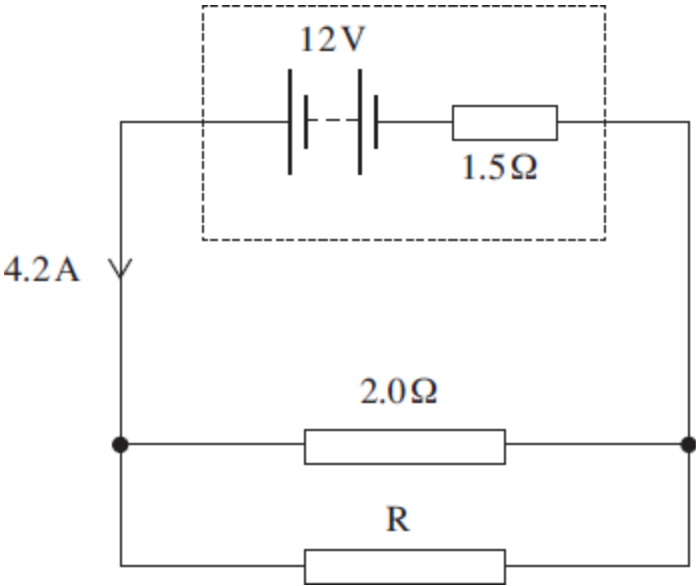The circuit diagram below shows a battery of electromotive force (emf) 12 V and internal resistance 1.5 Ω connected to a 2.0 Ω resistor in parallel with an unknown resistor, R. The battery supplies a current of 4.2 A.



(a) (i) Show that the potential difference (pd) across the internal resistance is 6.3 V.

(1)

(ii) Calculate the pd across the 2.0 Ω resistor.

pd _____ V

(1)

(iii) Calculate the current in the 2.0 Ω resistor.

current _____ A

(1)

(iv) Determine the current in R.

current _____ A

(1)

(v) Calculate the resistance of R.

R _____ Ω

(1)

(vi) Calculate the total resistance of the circuit.

circuit resistance _____ Ω

(2)

(b) The battery converts chemical energy into electrical energy that is then dissipated in the internal resistance and the two external resistors.

(i) Using appropriate data values that you have calculated, complete the following table by calculating the rate of energy dissipation in each resistor.

resistor	rate of energy dissipation / W
internal resistance	
2.0 Ω	
R	

(3)


(ii) Hence show that energy is conserved in the circuit.

(2)

(Total 12 marks)

3

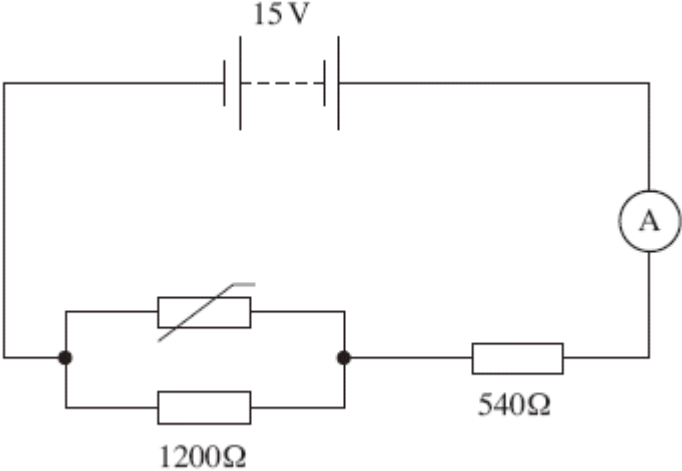The circuit shown below shows a thermistor connected in a circuit with two resistors, an ammeter and a battery of emf 15V and negligible internal resistance.



- (a) When the thermistor is at a certain temperature the current through the ammeter is 10.0 mA.
 - (i) Calculate the pd across the 540 Ω resistor.

answer = _____ V

(1)

- (ii) Calculate the pd across the 1200 Ω resistor.

answer = _____ V

(1)

(iii) Calculate the resistance of the parallel combination of the resistor and the thermistor.

answer = _____ Ω

(2)

(iv) Calculate the resistance of the thermistor.

answer = _____ Ω

(2)

(b) The temperature of the thermistor is increased so that its resistance decreases. State and explain what happens to the pd across the 1200 Ω resistor.

(3)

(Total 9 marks)


4

State what is meant by a superconductor.

(Total 1 mark)

5

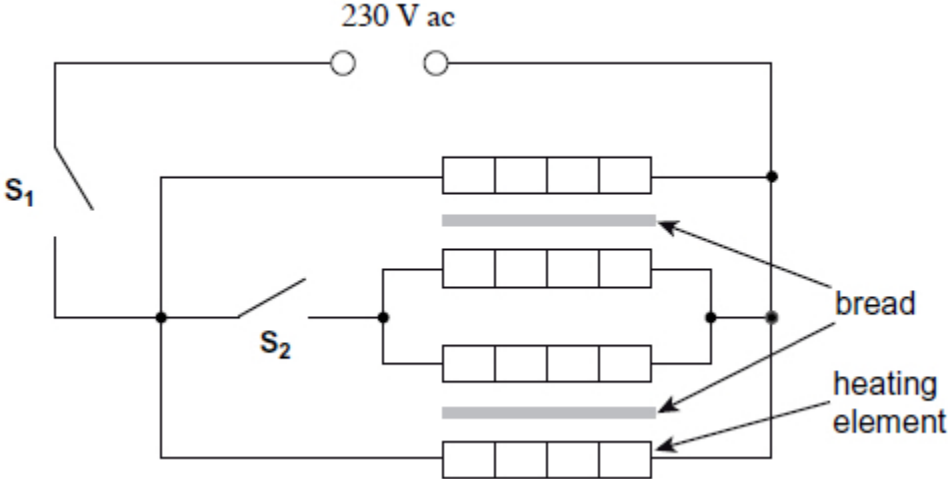The diagram shows the circuit diagram for a two-slice electric toaster that is operated at a mains voltage of 230 V.



The toaster has four identical heating elements and has two settings: normal and low. On the normal setting both sides of the bread are toasted. On the low setting, only one side of the bread is toasted. The setting is controlled by switches S_1 and S_2 .

The table shows the position of each switch and the power for each setting.

Setting	S_1	S_2	Power / W
Low	closed	open	400
Normal	closed	closed	800

(a) Calculate the current in S_2 when the normal setting is selected.

current _____ A

(2)

(b) (i) Show that the resistance of **one** heating element is approximately 260Ω when the toaster is operating at its working temperature.

(2)

(ii) Calculate the total resistance when the normal setting is selected.

resistance _____ Ω

(2)

(iii) Each heating element is made of nichrome wire of diameter 0.15 mm .
The nichrome wire is wrapped around an insulating board.

Determine the length of nichrome wire needed to provide a resistance of 260Ω .

resistivity of nichrome at the working temperature = $1.1 \times 10^{-6} \Omega \text{ m}$

length of wire _____ m

(3)

(c) Explain why the resistivity of the nichrome wire changes with temperature.

(3)

- (d) The nichrome wire has an equilibrium temperature of 174°C when the toaster is operating.
Calculate the peak wavelength of the electromagnetic radiation emitted by the wire.
Give your answer to an appropriate number of significant figures.

peak wavelength _____ m

(3)

(Total 15 marks)

6

A cordless phone handset contains two rechargeable cells connected in series. Each cell has an emf of 2.0 V and, when fully charged, the combination stores energy sufficient to provide 850 mA for 1 hour.

- (a) Calculate the total energy stored by the two cells when fully charged.

energy stored _____ J

(3)

- (b) The internal resistance of each cell is $0.60\ \Omega$.
Calculate the potential difference across the two cells when they are connected in series across a $20.0\ \Omega$ load.


potential difference _____ V

(3)

(Total 6 marks)

7

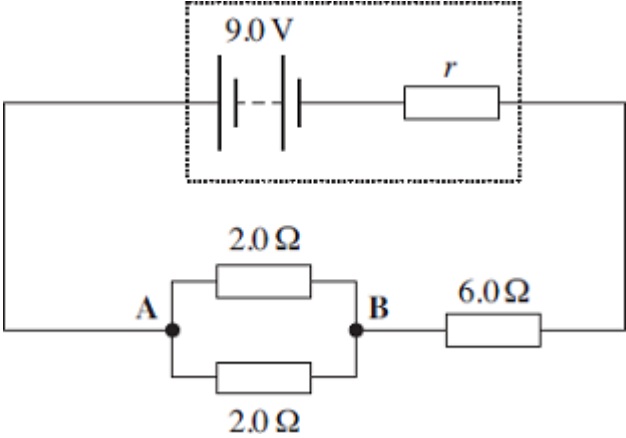A battery of emf 9.0 V and internal resistance, r , is connected in the circuit shown in the figure below.



- (a) The current in the battery is 1.0 A.
 - (i) Calculate the pd between points **A** and **B** in the circuit.

answer = _____ V (2)

- (ii) Calculate the internal resistance, r .

answer = _____ Ω (2)

- (iii) Calculate the **total** energy transformed by the battery in 5.0 minutes.

answer = _____ J (2)

- (iv) Calculate the percentage of the energy calculated in part (iii) that is dissipated in the battery in 5.0 minutes.

answer = _____ %

(2)

- (b) State and explain **one** reason why it is an advantage for a rechargeable battery to have a low internal resistance.

(2)

(Total 10 marks)

8

A car battery has an emf of 12 V and an internal resistance of $9.5 \times 10^{-3} \Omega$. When the battery is used to start a car the current through the battery is 420 A.

- (a) Calculate the voltage across the terminals of the battery, when the current through the battery is 420 A.

answer _____ V

(2)

- (b) The copper cable connecting the starter motor to the battery has a length of 0.75 m and cross-sectional area of $7.9 \times 10^{-5} \text{ m}^2$. The resistance of the cable is $1.6 \times 10^{-3} \Omega$.

Calculate the resistivity of the copper giving an appropriate unit.


answer _____

(3)

(Total 5 marks)

9

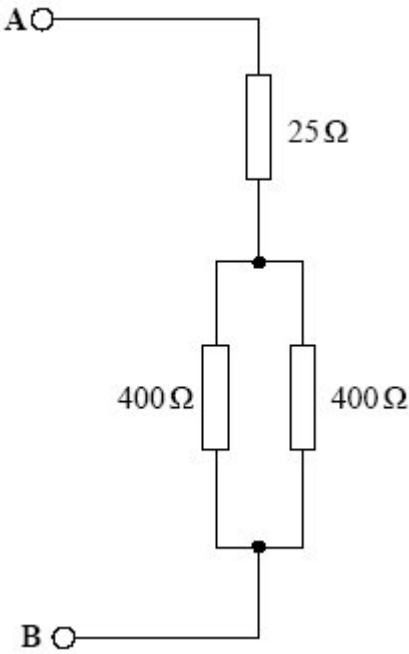The diagram below shows an arrangement of resistors.



(a) Calculate the total resistance between terminals **A** and **B**.

answer = _____ Ω

(2)

(b) A potential difference is applied between the two terminals, **A** and **B**, and the power dissipated in each of the $400\ \Omega$ resistors is $1.0\ \text{W}$.

(i) Calculate the potential difference across the $400\ \Omega$ resistors.

answer = _____ V

(ii) Calculate the current through the 25 Ω resistor.

answer = _____ A

(iii) Calculate the potential difference applied to terminals **A** and **B**.

answer = _____ V

(6)

(Total 8 marks)

10

When transmitting electricity, energy is lost owing to the resistance of the cables.

Calculate the resistance of 200 km of copper cable with cross-sectional area $1.5 \times 10^{-5} \text{ m}^2$.

resistivity of copper = $1.7 \times 10^{-8} \Omega \text{ m}$

resistance _____

(Total 3 marks)

11

The units of physical quantities can be expressed in terms of the fundamental (base) units of the SI system. In which line in the table are the fundamental units correctly matched to the physical quantity?

	Physical quantity	Fundamental units	
A	charge	A s^{-1}	<input type="checkbox"/>
B	power	$\text{kg m}^2 \text{s}^{-3}$	<input type="checkbox"/>
C	potential difference	$\text{kg m}^2 \text{s A}^{-1}$	<input type="checkbox"/>
D	energy	$\text{kg m}^2 \text{s}^{-1}$	<input type="checkbox"/>

(Total 1 mark)


12 When the temperature of a copper wire increases, its ability to conduct electricity

- A remains the same.
- B increases.
- C decreases.
- D remains the same at first and then increases.

(Total 1 mark)

13 The diagram shows a network of resistors connected between the terminals P and Q.

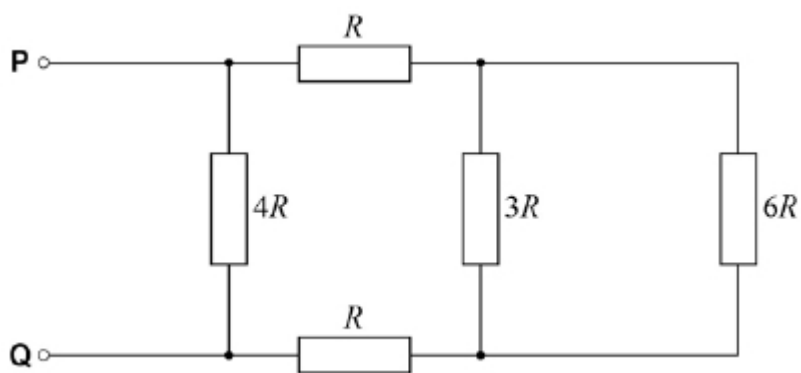The resistance of each resistor is shown.



What is the effective resistance between P and Q?

- A R
- B $2R$
- C $3R$
- D $4R$

(Total 1 mark)

14

A metal wire has a length l and a cross-sectional area A . When a potential difference V is applied to the wire, there is a current I in the wire.

What is the resistivity of the wire?

A $\frac{lA}{Vl}$

B $\frac{VA}{Il}$


C $\frac{Il}{VA}$

D $\frac{Vl}{lA}$

(Total 1 mark)

15

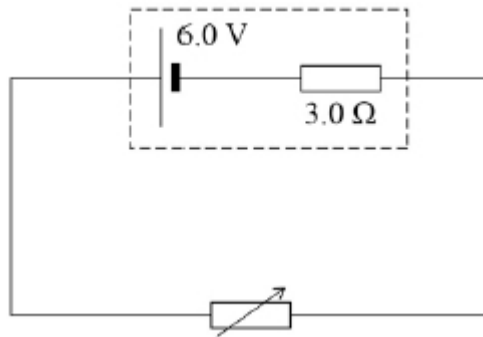The cell in the following circuit has an emf (electromotive force) of 6.0 V and an internal resistance of 3.0 Ω . The resistance of the variable resistor is set to 12 Ω .



How much electrical energy is converted into thermal energy **within the cell** in 1 minute?

A 0.48 J

B 29 J

C 45 J

D 144 J

(Total 1 mark)

16

Three identical cells, each of internal resistance R , are connected in series with an external resistor of resistance R . The current in the external resistor is I . If one of the cells is reversed in the circuit, what is the new current in the external resistor?

A $\frac{I}{3}$

B $\frac{4I}{9}$


C $\frac{I}{2}$

D $\frac{2I}{3}$

(Total 1 mark)

17

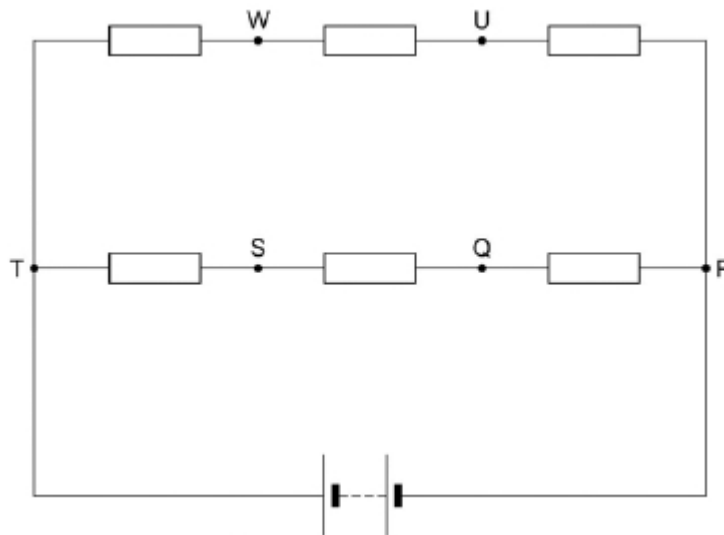In the circuit shown below, each of the resistors has the same resistance.



A voltmeter with very high resistance is connected between two points in the circuit.

Between which two points of connection would the voltmeter read zero?

A Q and U

B P and T

C Q and W

D S and U

(Total 1 mark)

Mark schemes

1

- (a) *(use of $R = \rho l/A$)*
 $A = 9.7 \times 10^{-8} \times 0.50/0.070 \checkmark$ 1
 $A = 6.929 \times 10^{-7} \text{ (m}^2\text{)} \checkmark$ 1
 diameter = $\sqrt{(6.929 \times 10^{-7} \times 4/\pi)} = 9.4 \times 10^{-4} \text{ (m)} \checkmark$
CE for third mark if incorrect area 1
- (b) $R = 1.5/0.66 = 2.3(\Omega) \text{ (2.27)} \checkmark$ 1
- (c) *(use of $V = IR$)*
 $I = 1.5/(22 + 1.2) = 0.065\checkmark\text{(A)} \text{ (0.0647)} \checkmark$ 1
- (d) current in $R_1 = 0.66 - 0.0647 = 0.595 \text{ (A)} \checkmark$
CE from 4.2/4.3 1
 resistance of R_1 and probe = $1.5/0.595 = 2.52 \text{ (}\Omega\text{)} \checkmark$
alternative method: $1/2.3 = 1/23.2 + 1/(R_{\text{probe}} + 2.4) \checkmark$ 1
 resistance of probe = $2.52 - 2.4 = 0.12 \text{ (}\Omega\text{)} \checkmark$
correct rearrangement \checkmark
range 0.1 – 0.15 \checkmark
accept 1 sig. fig. for final answer 1
- (e) cross-sectional area must decrease OR $R \propto 1/A$
indicated by downward arrow or negative sign which can be seen on answer line 1
 area decreases by 1.6% hence diameter must decrease by 0.8% \checkmark
accept 1% 1
- (f) ANY TWO FROM
 correct reference to lost volts OR terminal pd OR reduced current \checkmark
 reference to resistors not changing OR resistors constant ratio \checkmark
 reference to voltmeter having high/infinite resistance (so not affecting circuit) \checkmark
 reference to pd between AB being (very) small (due to closeness of resistance ratios in each arm) \checkmark
 voltmeter (may not be) sensitive enough \checkmark 1
 1

[12]

2

- (a) (i) *(use of $V=Ir$)*
 $V = 4.2 \times 1.5 \checkmark = 6.3 \text{ (V)}$

1

(ii) $pd = 12 - 6.3 = 5.7 \text{ V} \checkmark$
NO CE from (i)

1

(iii) (use of $I = V / R$)
 $I = 5.7 / 2.0 = 2.8(5) \text{ A} \checkmark$
CE from (ii)
(a(ii)/2.0)
accept 2.8 or 2.9

1

(iv) $I = 4.2 - 2.85 = 1.3(5) \text{ A} \checkmark$
CE from (iii)
(4.2 - (a)(iii))
accept 1.3 or 1.4

1

(v) $R = 5.7 / 1.35 = 4.2 \Omega \checkmark$
CE from (iv)
(a(ii) / (a)(iv))
Accept range 4.4 to 4.1

1

(vi) $\frac{1}{R_{\text{Parallel}}} = \frac{1}{4.2} + \frac{1}{2.0} = 0.737 \checkmark$

CE from (a)(v)

$R_{\text{parallel}} = 1.35 \Omega$

second mark for adding internal resistance

$R_{\text{total}} = 1.35 + 1.5 \checkmark = 2.85 \Omega$

OR

$R = 12/4.2 \checkmark$

$R = 2.85 \Omega \checkmark$

2

(b) (i)

resistor	Rate of energy dissipation (W)
1.5 Ω internal resistance	$4.2^2 \times 1.5 = 26.5 \checkmark$
2.0 Ω	$2.85^2 \times 2.0 = 16.2 (15.68 - 16.82) \checkmark$
R	$1.35^2 \times 4.2 = 7.7 (7.1 - 8.2) \checkmark$

CE from answers in (a) but not for first value

2.0: $a(\text{iii})^2 \times 2$

R: $a(\text{iv})^2 \times a(\text{v})$

3

- (ii) energy provided by cell per second = $12 \times 4.2 = \underline{50.4}$ (W) ✓
 energy dissipated in resistors per second = $26.5 + 16.2 + 7.7 = 50.4$ ✓
 (hence energy input per second equals energy output)
if not equal can score second mark if an appropriate comment

2

[12]

3

- (a) (i) voltage = $0.01 \times 540 = 5.4$ V (1)

1

- (ii) voltage = $15 - 5.4 = 9.6$ V (1)

1

- (iii) (use of resistance = voltage/current)

resistance = $9.6/0.01$ (1) = 960Ω (1)

or $R_T = 15/0.01 = 1500 \Omega$ (1)

$R = 150 - 590 = 960 \Omega$ (1)

or potential divider ratio (1)(1)

2

- (iv) (use of $1/R = 1/R_1 + 1/R_2$)

$1/960 = 1/200 + 1/R_2$ (1)

$1/R_2 = 1/960 - 1/1200$

$R_2 = 4800 \Omega$ (1)

2

- (b) (voltage of supply constant)

(circuit resistance decreases)

(supply) current increases or potential divider argument (1)

hence pd across 540Ω resistor increases (1)

hence pd across 1200Ω decreases (1)

or resistance in parallel combination decreases (1)

pd across parallel resistors decreases (1)

pd across 1200Ω decreases (1)

3

[9]

4

Resistance is zero at (or below) critical temperature

"Negligible resistance" is insufficient

[1]

- 5** (a) Correct substitution into $P=VI$
1.74 (A) 2
- (b) (i) Correct substitution into $R=V/I$ or V^2/P or P/I^2
264 (Ω)
Allow correct use of parallel resistor equation 2
- (ii) Use of $1/R_T = 1/R_1 + 1/R_2$ or $R = V^2/P$
65 (66.1) (Ω) 2
- (iii) $A = \pi(1.5 \times 10^{-4})^2/4$ or $\pi(7.5 \times 10^{-5})^2$ or 1.767×10^{-8} (m^2)
Substitution into $l=RA/\rho$ with their area
4.2 (4.18) (m)
2 marks for 17 (m), using of d instead of r 3
- (c) Resistivity / resistance increases with increasing temperature
(Lattice) ions vibrate with greater amplitude
Rate of movement of charge carriers / electrons (along wire)
reduced (for given pd)
ORA
Condone atoms for ions.
Accept "vibrate more".
Accept more frequent collisions occur between electrons and ions
owtte 3
- (d) $2.9 \times 10^{-3}/447$ or $2.9 \times 10^{-3}/174$ seen
 6.5 (6.49) $\times 10^{-6}$ (m)
Correct answer given to 2 sig fig
Condone use of 174 for T for C1 and B1 marks
Allow 3 sig fig answer if 2.90×10^{-3} used 3

[15]

- 6** (a) use of $E = ItV$ (or equivalent) or substitution into equation irrespective of powers of 10 **C1**
- allow 2 for 6120 (J)*
- emf = 4.0 V **C1**
- 1.22×10^4 J **A1**

3

(b) Internal resistance = 1.2 (Ω)

C1

allow 2 for 0.22(6) V

Current calculated (0.19 A) or potential divider formula used 3.7(7) V

C1

A1

3

[6]

7

(a) (i) (use of $V = IR$)

$$R_{\text{total}} = 1 \text{ (ohm)} \checkmark$$

$$V = 1 \times 1 = 1.0 \text{ V} \checkmark$$

2

(ii) (use of $V = IR$)

$$R = 9.0/1.0 = 9.0 \Omega \checkmark$$

$$r = 9.0 - 1.0 - 6.0 = 2.0 \Omega \checkmark$$

or use of ($E = I(R + r)$)

$$9.0 = 1(7 + r) \checkmark$$

$$r = 9.0 - 7.0 = 2.0 \Omega \checkmark$$

2

(iii) (use of $W = VIt$)

$$W = 9.0 \times 1.0 \times 5 \times 60 \checkmark$$

$$W = 2700 \text{ J} \checkmark$$

2

(iv) energy dissipated in internal resistance = $I^2 \times 2.0 \times 5 \times 60 = 600 \text{ (J)}$ \checkmark

$$\text{percentage} = 100 \times 600/2700 = 22\% \checkmark \text{ CE from part aii}$$

2

- (b) internal resistance limits current ✓
 hence can provide higher current ✓
 or energy wasted in internal resistance/battery ✓
 less energy wasted (with lower internal resistance) ✓
 or charges quicker ✓
 as current higher or less energy wasted ✓
 or (lower internal resistance) means higher terminal pd/voltage ✓
 as less pd across internal resistance or mention of lost volts ✓

2

[10]

8

- (a) (use of $E = V + Ir$)

$$12 = V + 420 \times 0.0095 \text{ (1)}$$

$$V = 8.0(1)V \text{ (1)}$$

2

- (b) $\rho = RA/l = 1.6 \times 10^{-3} \times 7.9 \times 10^{-5}/0.75 \text{ (1)}$

$$R = 1.7 \times 10^{-7} \text{ (1) } \Omega\text{m (1)}$$

3

[5]

9

- (a) (use of $1/R_{\text{total}} = 1/R_1 + 1/R_2$)

$$1/R_{\text{total}} = 1/400 + 1/400 = 2/400$$

$$R_{\text{total}} = 200 \Omega \text{ (1) (working does not need to be shown)}$$

$$\text{hence total resistance} = 25 + 200 = 225\Omega \text{ (1)}$$

2

- (b) (i) (use of $P = V^2/R$)

$$1 = V^2/400 \text{ (1)}$$

$$V^2 = 400 \text{ (working does not need to be shown)}$$

$$V = 20V \text{ (1)}$$

- (ii) (use of $I = V/R$)

$$I = 20/400 = 0.05A \text{ (1) (working does not need to be shown)}$$

$$\text{hence current} = 2 \times 0.05 = 0.10A \text{ (1)}$$

(iii) (use of $V = IR$)

pd across 25Ω resistor = $25 \times 0.10 = 2.5\text{V}$ (1)
(working does not need to be shown)

hence maximum applied pd = $20 + 2.5 = 22.5\text{V}$ (1)

6

[8]

10 use of $R = \frac{\rho l}{A}$ (1)

227 (1)

Ω (1)

[3]

11 B

[1]

12 C

[1]

13 B

[1]

14 B

[1]

15 B

[1]

16 A

[1]

17 A

[1]

Examiner reports

1 Experience from past physics exams at this level indicates that students are better at answering quantitative questions involving electric circuits and this is supported by evidence from this question where the calculations were frequently done well. Part (a) required students to calculate the diameter of the wire and a high proportion of students were able to do this successfully. Full marks were obtained by over 70% of students. There was more variation in parts (b), (c) and (d). While the majority of students were able to calculate the resistance of the circuit, analysing the parallel arrangement was more discriminating. In particular, calculating the resistance of the probe proved challenging. A common mistake was the assumption that the current divided equally in the two branches and therefore the current in the probe was the same as that calculated for R3. Many students found (e) difficult and tried to determine the percentage change in diameter using extended calculations which frequently led to arithmetic errors. The first mark was for recognition that the diameter must decrease and any indication of this such as a downward arrow or negative sign was accepted. The marks obtained for part (f) were disappointing in spite of the mark scheme being expanded to accept a greater range of answers. Very few students picked up that the question referred to the voltmeter reading rather than the pd between A and B. The first marking point was for explaining the effect the internal resistance would have on the circuit by for example reducing the current or terminal pd. The second mark was for a sensible suggestion explaining why the voltmeter reading did not change such as realizing that the closeness of the resistance ratios would make the pd being measured very small. Having the bridge circuit slightly off balance did mean that a comment on the high resistance of the voltmeter was relevant and some did identify this point.

2 Part (a) was highly structured and led candidates through a full circuit calculation in stages. This approach appeared to have helped them and more successful solutions were seen than has been the case in the past with this type of circuit.

The part that caused the most problems was (a) (ii) with a significant proportion of candidates not appreciating that the pd across the 2.0Ω resistor was the same as that across resistor R. Candidates were however, not penalized when they carried their incorrect answer to subsequent parts and consequently the remaining calculations were often carried out successfully.

Part (b) proved to be much more demanding and only about half the candidates managed to complete the table for the rate of energy dissipation successfully.

The demonstration of energy conservation in part (b) (ii) provided an even greater challenge and only about a third of candidates provided a convincing analysis of energy conservation in the circuit. A fifth of candidates made no attempt at this part of the question.

3 This question proved to be very discriminating with only the more able candidates able to score high marks. The calculations involved in part (a) proved too challenging for many candidates. Part (a) (i) and (ii) generated the most correct responses, but the remainder of the analysis was only accessible to the more able candidates.

Part (b) required analysis without calculation and the majority of explanations seen were confused and not self consistent. Many candidates stated that more current goes through the thermistor and therefore the pd across it falls, resulting in the pd across the parallel 1200Ω resistor increasing. Another common misunderstanding was the effect that the decreasing thermistor resistance had on the current through the battery. Many thought that the current remained constant and, although this still led them to deduce that the pd fell, their arguments frequently contained contradictions.

4 Students needed to use the term “critical temperature” in their definition.

- 5
- (a) Most students obtained the total current but failed to appreciate the need to halve this value.
 - (b) A variety of routes were possible for part (i) but clear evidence of the method was expected to be seen. The ‘parallel resistor’ equation was often invoked but rarely written explicitly. Parts (ii) and (iii) were answered well.
 - (c) This was poorly answered. Explanations often lacked the required precision. Many students clearly thought that nichrome is a semi-conductor.
 - (d) Most students recognised the need to use Wien’s Law and to convert the temperature to kelvin.

6 It was common for candidates to use an emf of 2.0 V in (a) but most correctly used the relationship of energy = emf × current × time. A minority of candidates used a time of 60 s rather than the correct 3600 s and a few misinterpreted 850 mA.

In (b) it was common for candidates to use the 850 mA given in (a) as the current; few calculated the correct current (or to correctly use the potential divider formula) and of those that did about half went on to find the ‘lost volts’ rather than the terminal pd.

7 Students fared better in the circuit analysis involved in this question than they did in question 6. Parts (a) (i), (ii) and (iii) were answered well with a significant proportion of students able to correctly find the total circuit resistance. The calculation of the parallel network was done correctly by the majority of students, although the working shown by many was sometimes not set out properly with the reciprocal of total resistance being equated to the total resistance. This was in part due to the combined resistance being equal to 1 Ω.

Part (a) (iv), in which students had to calculate the energy transformed by the battery in 5.0minutes, was not answered as well. A significant proportion of students did not appreciate that this was found by multiplying the emf of the battery by the appropriate time. Part (a) (v) caused students even more problems and only a minority of the more able students were able to correctly calculate the energy dissipated in the internal resistance of the battery.

The final part of this question was well answered with most students giving sensible suggestions. However, one out of two marks was quite common due to students mixing up an explanation with a reason; an example being ‘has a higher terminal pd’ and ‘provides large current’.

8 Part (a) caused similar problems to the question on emf and internal resistance in the January examination. A common, incorrect approach was to calculate the potential difference across the internal resistance and quote this as the value of terminal pd.

Part (b) proved to be much more accessible and the calculation only caused a few candidates problems. The unit for resistivity does confuse a significant proportion of candidates and this is often quoted as $\Omega \text{ m}^{-1}$ or Ω/m .

9 Part (a) was answered well, with many candidates obtaining full marks.

Part (b) caused more problems and the use of the power formula that involves potential difference and resistance was quite rare. In part (b) (ii) there was some confusion over potential difference and candidates frequently used their answer from part (b) (i). Part (b) (iii) was answered much better, with candidates frequently benefiting from consequential error.